



**Sri Lanka Institute of Information Technology**

**Faculty of Engineering**

**Analogue Electronics - EC2140**

**DC Power Supply Design**

**Assignment 01**

Name: Jayasinghe J.M.K.D.

Index: EN21452970

## Continuous Assessment Cover Sheet

### Faculty of Engineering

| Module Details      |        |                         |                      |
|---------------------|--------|-------------------------|----------------------|
| Module Code         | EC2140 | Module Title            | Analogue Electronics |
| Program: SLIIT      |        | Course: BSc engineering |                      |
| Stream: Electronics |        |                         |                      |

| Assessment details   |                        |                     |            |
|----------------------|------------------------|---------------------|------------|
| Title                | DC Power Supply Design | Group assignment    | NO         |
|                      |                        | If yes, Group No.   |            |
| Lecturer/ Instructor |                        | Date of Performance | 20/10/2022 |
| Due date             | 28/10/2022             | Date submitted      | 26/10/2022 |

| Student statement and signature   |                                      |                                      |            |                     |  |
|---|--------------------------------------|--------------------------------------|------------|---------------------|--|
| <p>By this declaration, I/we confirm my/our understanding and acceptance that the work reported in this report is my/our own work. I/we also understand the consequences of engaging in plagiarism or copying others work without proper citation. Any material used in this work (whether from published sources, the internet or elsewhere) have been fully acknowledged and referenced and are without fabrication or falsification of data.</p> <p>[Copying or plagiarism will result in a "0" mark for the continuous assessment and "F" for the module after an investigation on academic misconduct;</p> <p>All academic misconduct is considered seriously and defined as dishonest and in direct opposition to the values of a learning community. Misconduct may result in penalties from failure to exclusion from the campus. Further help and guidance on how to avoid academic misconduct can be obtained from your academic advisor/tutor]</p> <p>By this declaration, I/we confirm my understanding and acceptance that-</p> <ul style="list-style-type: none"> <li>I/we have adhered to relevant ethical guidelines and procedures in the completion of the assignment.</li> <li>I/we have not allowed another student to have access to or copy from this work.</li> <li>This work has not been submitted previously.</li> </ul> <p>[The Institute may request an electronic copy of this work for submission to the Plagiarism detection facility (TURNITIN). You must make sure that an electronic copy of your work is available in these circumstances]</p> |                                      |                                      |            |                     |  |
| Details of the student/s submitting the assignment  | Signature                            |                                      |            |                     |  |
| <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <th style="width: 25%;">ID Number</th> <th style="width: 75%;">Name (As per the institute records )</th> </tr> <tr> <td>EN21452970</td> <td>Jayasinghe J.M.K.D.</td> </tr> </table>   | ID Number                            | Name (As per the institute records ) | EN21452970 | Jayasinghe J.M.K.D. |  |
| ID Number   | Name (As per the institute records ) |                                      |            |                     |  |
| EN21452970  | Jayasinghe J.M.K.D.                  |                                      |            |                     |  |

#### OFFICE USE ONLY

|  |   |  |
|--|---|--|
| <b>Receiving Officer</b><br><small>(seal, signature, date)</small> | <b>Specific comments about the work (including overall comments and guidelines for improvement)</b> |  |
|  | <b>Tutor:</b>   | <b>Signature:</b>  |
|  | <b>Marks:</b><br><small>examinations]</small>   | <small>[ All marks are subject to external moderation and approval of board of</small> |

# Assignment 1: DC Power Supply Design

- **INTRODUCTION**

Due to economic considerations of electric power, electric power is generated, transmitted and distributed almost exclusively in AC form, but many electronic devices and circuits require DC supply to operate. Batteries and dry cells are suitable for this use. They are portable and have no ripple, but their voltages are low, they require frequent replacement, and they are more expensive than standard dc power supply. For this reason, DC power supplies is required to convert AC electricity into DC.



- **Purpose**

Set up the circuit and get an understanding of the circuit and to provide power to the amplifier circuit.

- **Activity**


Using the domestic supply voltage of 230 V, to create a power supply as the rated output voltage = 12V and the maximum output current = 500 mA and the ripple factor < 5%.

- The designing of the circuit was divided into 04 parts.

1. Step Down Transformer
2. Full Wave Bridge
3. Capacitor
4. Zener Regulator


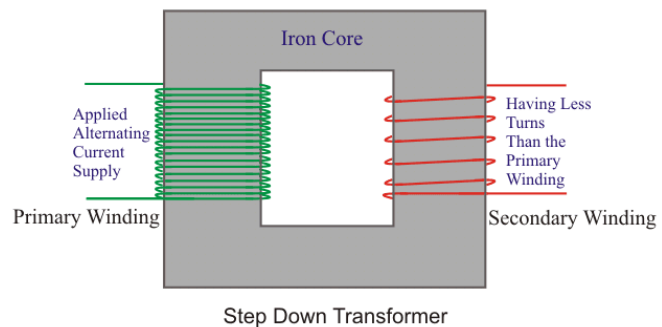
## 1. Step Down Transformer

A step-down transformer is a transformer that changes the voltage at the primary and secondary windings from high to low. In terms of coil windings, the primary winding of a step-down transformer has more turns than the secondary winding. In this operation, a step-down transformer is used which reduces 230 V to 15 V.



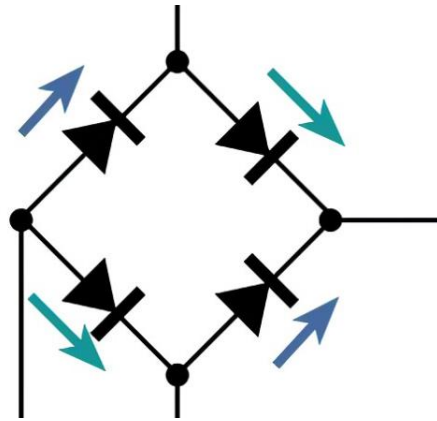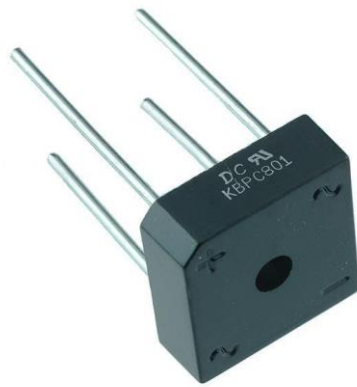
## 2. Bridge rectifier

Bridge rectifiers are a specific kind of full-wave rectifier that effectively transforms AC current into DC current by employing four or more diodes in a bridge circuit design. In this activity, 4 1N4007 diodes have been used to create the bridge rectifier.



Bridge Rectifier Diode

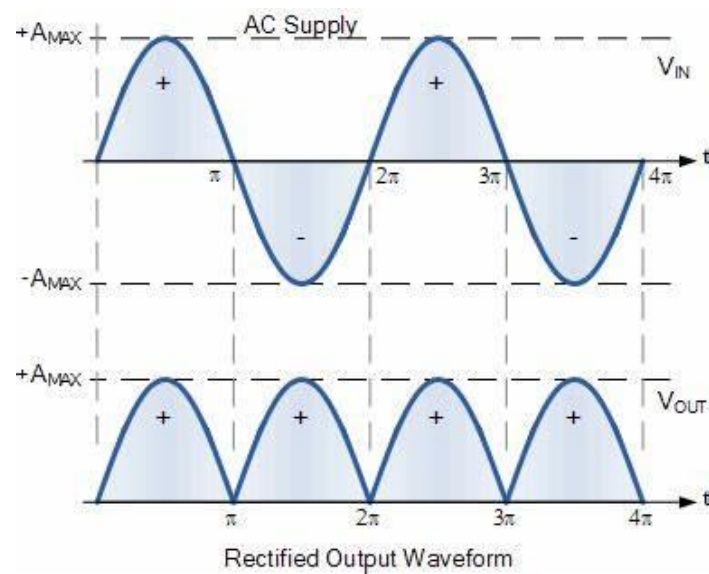The output wave form can be observed as bellow after implementing bridge rectifier.



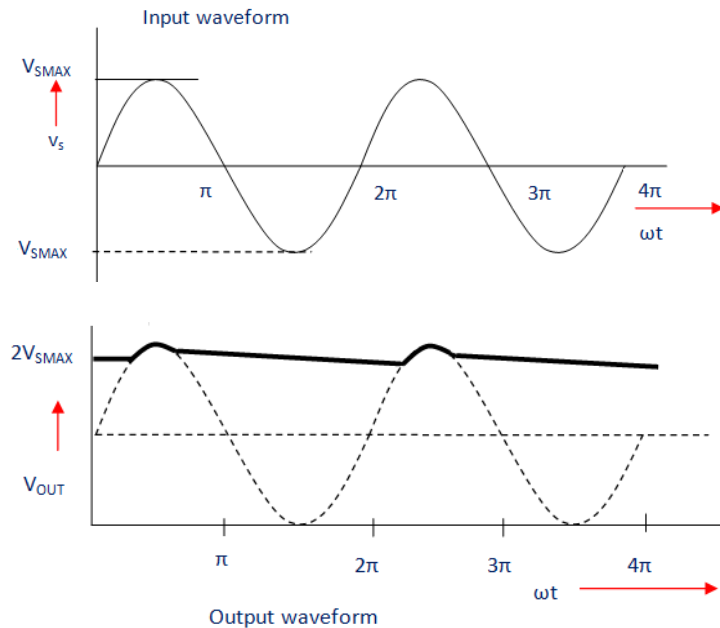
### 3. Capacitor

Capacitor is a device for storing electrical energy, consisting of two conductors in proximity and insulated from each other. capacitor is used to smooth the sine curve. Also, when the capacity of the capacitor increases, the smoothness of the sine curve increases. Then perfect DC current can be obtained. The capacitor used in this activity is a 4.7 mF capacitor.



The output wave form can be observed as bellow after capacitance.



#### 4. Zener regulator

A Zener regulator is an electrical circuit that maintains a constant DC output voltage using a Zener diode. When the Zener diode receives a voltage higher than the breakdown voltage, the Zener diode reverses bias and causes current to flow through the diode, maintaining the potential gap on both sides of the Zener at a constant value. A 12 V zener diode has been used here.



## • DESIGN PROCEDURE


### I. Design Specifications

- The input of the power supply is the domestic supply which is  $230\text{ V} \pm 5\%$ .
- The parameter values of power supply are as given below.

| Parameter              | Expected Value/Range |
|------------------------|----------------------|
| Rated output voltage   | 12 V                 |
| Maximum output current | 500 mA               |
| Ripple factor          | 5% Maximum           |

The step-down transformer was used as first step to minimize domestic power voltage to 15 V. Then, using 4 1N4007 diodes as the full wave bridge that AC waveform was converted into the full wave form. After that, a capacitor was used to get a smooth waveform. Finally, the Zener regulator was used to keep the constant output value of 12 V voltage.

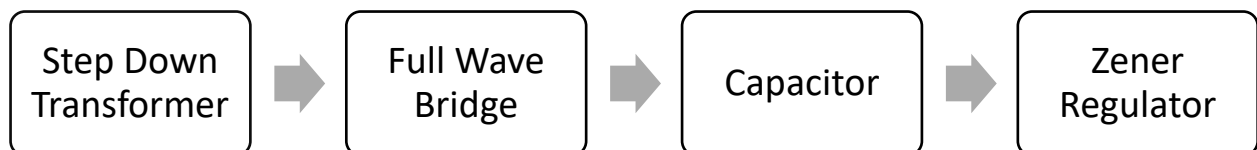
- Block diagram of the implemented circuit


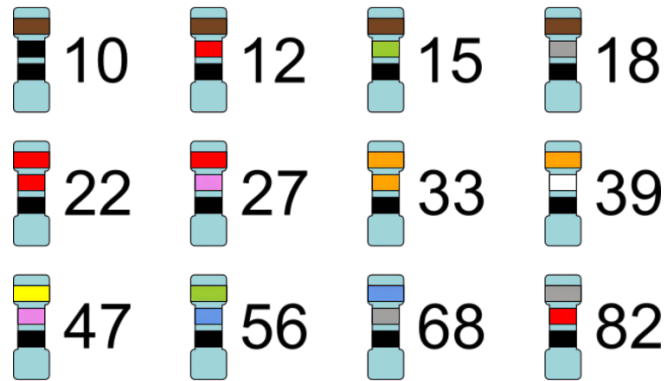
### II. Data References

- Resistor

According to the E12 resistor series,  $10\ \Omega$  and  $22\ \Omega$  were chosen as the two resistors needed to set up this circuit.



- Capacitor

According to the standard capacitor values, 4.7 mF was chosen as the capacitor needed to set up this circuit.

| These fixed capacitor values are the most commonly found |    |     |      |       |      |     |    |     |      |        |
|--|----|-----|------|-------|------|-----|----|-----|------|--------|
| pF   | pF | pF  | pF   | μF    | μF   | μF  | μF | μF  | μF   | μF     |
| 1.0  | 10 | 100 | 1000 | 0.01  | 0.1  | 1.0 | 10 | 100 | 1000 | 10,000 |
| 1.1  | 11 | 110 | 1100 |       |      |     |    |     |      |        |
| 1.2  | 12 | 120 | 1200 |       |      |     |    |     |      |        |
| 1.3  | 13 | 130 | 1300 |       |      |     |    |     |      |        |
| 1.5  | 15 | 150 | 1500 | 0.015 | 0.15 | 1.5 | 15 | 150 | 1500 |        |
| 1.6  | 16 | 160 | 1600 |       |      |     |    |     |      |        |
| 1.8  | 18 | 180 | 1800 |       |      |     |    |     |      |        |
| 2.0  | 20 | 200 | 2000 |       |      |     |    |     |      |        |
| 2.2  | 22 | 220 | 2200 | 0.022 | 0.22 | 2.2 | 22 | 220 | 2200 |        |
| 2.4  | 24 | 240 | 2400 |       |      |     |    |     |      |        |
| 2.7  | 27 | 270 | 2700 |       |      |     |    |     |      |        |
| 3.0  | 30 | 300 | 3000 |       |      |     |    |     |      |        |
| 3.3  | 33 | 330 | 3300 | 0.033 | 0.33 | 3.3 | 33 | 330 | 3300 |        |
| 3.6  | 36 | 360 | 3600 |       |      |     |    |     |      |        |
| 3.9  | 39 | 390 | 3900 |       |      |     |    |     |      |        |
| 4.3  | 43 | 430 | 4300 |       |      |     |    |     |      |        |
| 4.7  | 47 | 470 | 4700 | 0.047 | 0.47 | 4.7 | 47 | 470 | 4700 |        |
| 5.1  | 51 | 510 | 5100 |       |      |     |    |     |      |        |
| 5.6  | 56 | 560 | 5600 |       |      |     |    |     |      |        |
| 6.2  | 62 | 620 | 6200 |       |      |     |    |     |      |        |
| 6.8  | 68 | 680 | 6800 | 0.068 | 0.68 | 6.8 | 68 | 680 | 6800 |        |
| 7.5  | 75 | 750 | 7500 |       |      |     |    |     |      |        |
| 8.2  | 82 | 820 | 8200 |       |      |     |    |     |      |        |
| 9.1  | 91 | 910 | 9100 |       |      |     |    |     |      |        |

- Diode

Here, used 4 1N4007 diodes.



- Zener

Suitable Zener diode was 12 V / 1W.

| <b>ELECTRICAL CHARACTERISTICS</b> ( $T_{amb} = 25^{\circ}\text{C}$ , unless otherwise specified) |                                    |              |           |                         |     |  |                       |                         |
|--|------------------------------------|--------------|-----------|-------------------------|-----|--|-----------------------|-------------------------|
| PART NUMBER  | ZENER VOLTAGE RANGE <sup>(1)</sup> | TEST CURRENT |           | REVERSE LEAKAGE CURRENT |     | DYNAMIC RESISTANCE<br>$f = 1\text{ kHz}$ |                       | TEMPERATURE COEFFICIENT |
|  | $V_Z$ at $I_{ZT1}$                 | $I_{ZT1}$    | $I_{ZT2}$ | $I_R$ at $V_R$          |     | $Z_Z$ at $I_{ZT1}$ <sup>(1)</sup>        | $Z_{ZK}$ at $I_{ZT2}$ | $\alpha_{VZ}$           |
|  | V                                  | mA           |           | $\mu\text{A}$           | V   | $\Omega$                                 |                       | %/K                     |
|  | NOM.                               |              |           | MAX.                    |     | MAX.                                     | MAX.                  | TYP.                    |
| 1N5221   | 2.4                                | 20           | 0.25      | 100                     | 1   | 30                                       | 1200                  | - 0.085                 |
| 1N5222   | 2.5                                | 20           | 0.25      | 100                     | 1   | 30                                       | 1250                  | - 0.085                 |
| 1N5223   | 2.7                                | 20           | 0.25      | 75                      | 1   | 30                                       | 1300                  | - 0.08                  |
| 1N5224   | 2.8                                | 20           | 0.25      | 75                      | 1   | 30                                       | 1400                  | - 0.08                  |
| 1N5225   | 3                                  | 20           | 0.25      | 50                      | 1   | 29                                       | 1600                  | - 0.075                 |
| 1N5226   | 3.3                                | 20           | 0.25      | 25                      | 1   | 28                                       | 1600                  | - 0.07                  |
| 1N5227   | 3.6                                | 20           | 0.25      | 15                      | 1   | 24                                       | 1700                  | - 0.065                 |
| 1N5228   | 3.9                                | 20           | 0.25      | 10                      | 1   | 23                                       | 1900                  | - 0.06                  |
| 1N5229   | 4.3                                | 20           | 0.25      | 5                       | 1   | 22                                       | 2000                  | 0.055                   |
| 1N5230   | 4.7                                | 20           | 0.25      | 5                       | 2   | 19                                       | 1900                  | 0.03                    |
| 1N5231   | 5.1                                | 20           | 0.25      | 5                       | 2   | 17                                       | 1600                  | 0.03                    |
| 1N5232   | 5.6                                | 20           | 0.25      | 5                       | 3   | 11                                       | 1600                  | 0.038                   |
| 1N5233   | 6                                  | 20           | 0.25      | 5                       | 3.5 | 7  | 1600                  | 0.038                   |
| 1N5234   | 6.2                                | 20           | 0.25      | 5                       | 4   | 7  | 1000                  | 0.045                   |
| 1N5235   | 6.8                                | 20           | 0.25      | 3                       | 5   | 5  | 750                   | 0.05                    |
| 1N5236   | 7.5                                | 20           | 0.25      | 3                       | 6   | 6  | 500                   | 0.058                   |
| 1N5237   | 8.2                                | 20           | 0.25      | 3                       | 6.5 | 8  | 500                   | 0.062                   |
| 1N5238   | 8.7                                | 20           | 0.25      | 3                       | 6.5 | 8  | 600                   | 0.065                   |
| 1N5239   | 9.1                                | 20           | 0.25      | 3                       | 7   | 10                                       | 600                   | 0.068                   |
| 1N5240   | 10                                 | 20           | 0.25      | 3                       | 8   | 17                                       | 600                   | 0.075                   |
| 1N5241   | 11                                 | 20           | 0.25      | 2                       | 8.4 | 22                                       | 600                   | 0.076                   |
| 1N5242   | 12                                 | 20           | 0.25      | 1                       | 9.1 | 30                                       | 600                   | 0.077                   |
| 1N5243   | 13                                 | 9.5          | 0.25      | 0.5                     | 9.9 | 13                                       | 600                   | 0.079                   |
| 1N5244   | 14                                 | 9            | 0.25      | 0.1                     | 10  | 15                                       | 600                   | 0.082                   |
| 1N5245   | 15                                 | 8.5          | 0.25      | 0.1                     | 11  | 16                                       | 600                   | 0.082                   |
| 1N5246   | 16                                 | 7.8          | 0.25      | 0.1                     | 12  | 17                                       | 600                   | 0.083                   |
| 1N5247   | 17                                 | 7.4          | 0.25      | 0.1                     | 13  | 19                                       | 600                   | 0.084                   |
| 1N5248   | 18                                 | 7            | 0.25      | 0.1                     | 14  | 21                                       | 600                   | 0.085                   |
| 1N5249   | 19                                 | 6.6          | 0.25      | 0.1                     | 14  | 23                                       | 600                   | 0.086                   |
| 1N5250   | 20                                 | 6.2          | 0.25      | 0.1                     | 15  | 25                                       | 600                   | 0.086                   |
| 1N5251   | 22                                 | 5.6          | 0.25      | 0.1                     | 17  | 29                                       | 600                   | 0.087                   |
| 1N5252   | 24                                 | 5.2          | 0.25      | 0.1                     | 18  | 33                                       | 600                   | 0.088                   |
| 1N5253   | 25                                 | 5            | 0.25      | 0.1                     | 19  | 35                                       | 600                   | 0.089                   |
| 1N5254   | 27                                 | 4.6          | 0.25      | 0.1                     | 21  | 41                                       | 600                   | 0.09                    |
| 1N5255   | 28                                 | 4.5          | 0.25      | 0.1                     | 21  | 44                                       | 600                   | 0.091                   |
| 1N5256   | 30                                 | 4.2          | 0.25      | 0.1                     | 23  | 49                                       | 600                   | 0.091                   |
| 1N5257   | 33                                 | 3.8          | 0.25      | 0.1                     | 25  | 58                                       | 700                   | 0.092                   |
| 1N5258   | 36                                 | 3.4          | 0.25      | 0.1                     | 27  | 70                                       | 700                   | 0.093                   |
| 1N5259   | 39                                 | 3.2          | 0.25      | 0.1                     | 30  | 80                                       | 800                   | 0.094                   |
| 1N5260   | 43                                 | 3            | 0.25      | 0.1                     | 33  | 93                                       | 900                   | 0.095                   |
| 1N5261   | 47                                 | 2.7          | 0.25      | 0.1                     | 36  | 105                                      | 1000                  | 0.095                   |
| 1N5262   | 51                                 | 2.5          | 0.25      | 0.1                     | 39  | 125                                      | 1100                  | 0.096                   |
| 1N5263   | 56                                 | 2.2          | 0.25      | 0.1                     | 43  | 150                                      | 1300                  | 0.096                   |
| 1N5264   | 60                                 | 2.1          | 0.25      | 0.1                     | 46  | 170                                      | 1400                  | 0.097                   |
| 1N5265   | 62                                 | 2            | 0.25      | 0.1                     | 47  | 185                                      | 1400                  | 0.097                   |
| 1N5266   | 68                                 | 1.8          | 0.25      | 0.1                     | 52  | 230                                      | 1600                  | 0.097                   |
| 1N5267   | 75                                 | 1.7          | 0.25      | 0.1                     | 56  | 270                                      | 1700                  | 0.098                   |

### III. Analysis steps

- Domestic supply voltage is  $230 \text{ V} \pm 5\%$ . Voltage range is from  $241.5 \text{ V}$  to  $218.5 \text{ V}$ .

#### • Capacitor Value

$$\text{Ripple factor} = \frac{V_{r(\text{rms})}}{V_D} ; V_{r(\text{rms})} = \frac{V_{r(\text{pk-pk})}}{2\sqrt{3}} ;$$

$$\therefore \text{Ripple factor} = \frac{V_L}{R_{fc}} \times \frac{1}{V_{Dc}} \times \frac{1}{2\sqrt{3}} \quad V_{r(\text{pk-pk})} = \frac{I_c}{f_c} = \frac{V_L}{R_{fc}}$$

Ripple factor should be  $\leq 5\%$

$$\frac{1}{22 \times 100 \times 2\sqrt{3}} \leq 0.05$$

$$C \geq \frac{1}{22 \times 5 \times 2\sqrt{3}}$$

$$C \geq 2.6 \text{ mF}$$


chose,  $C = 3.3 \text{ mF}$

#### • $R_s$ resistor Value

$$V_{z,\text{min}} = V_{in,\text{min}} - 2V_r - V_{\text{ripple,max}} ; V_{\text{ripple,max}} = \frac{I_{\text{max}}}{f_c}$$

$$= 15\sqrt{2} \times 0.95 - (0.7)2 - \frac{500 \times 10^{-3}}{100 \times 3.3 \times 10^{-3}}$$
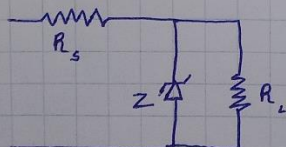
$$\underline{V_{z,\text{min}} = 17.24 \text{ V}}$$



Removing Zener diode.

$$V_{out,\text{min}} = V_{z,\text{min}} - I_{\text{max}} R_s \geq 12$$

$$17.24 - 500 \times 10^{-3} R_s \geq 12$$

$$R_s \leq 10.47 \Omega$$

chose,  $R_s = 10 \Omega$


- Zener power value

$$\begin{aligned}
 I_Z &= I - I_L \\
 I_{Z, \max} &= I_{\max} - I_{L, \min} \\
 &= \frac{V_{in, \max} - V_Z}{R_s} - I_{L, \min} = 0 \quad ; \quad V_{in, \max} = (15\sqrt{2} \times 1.05) - (0.7)2 \\
 &= \frac{20.87 - 12}{10} \quad = 20.87 \text{ V} \\
 I_{Z, \max} &= \underline{\underline{0.89 \text{ A}}} \\
 \text{power rating of zener diode} &= I_{Z, \max} V_Z \\
 &= 0.89 \times 12 \\
 P_Z &= \underline{\underline{10.68 \text{ W}}}
 \end{aligned}$$


#### IV. Simulation results
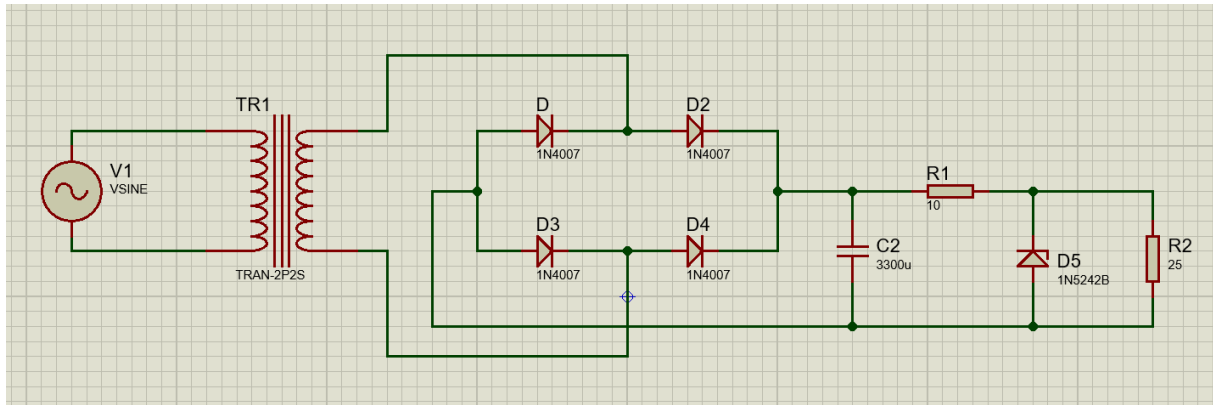
##### ➤ Schematic Design


Schematic Design was done by Proteus' software. The components used for that were diode, capacitor, resistor, step down transformer, AC current source, Zener diode etc.



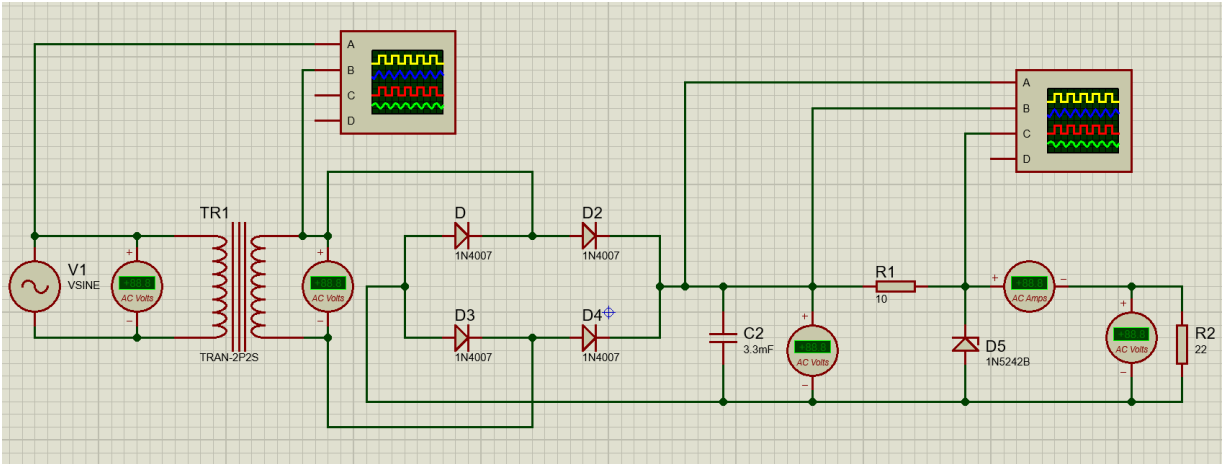- To get the voltage measurements, voltmeters and Oscilloscopes was set up.




- Simulation results

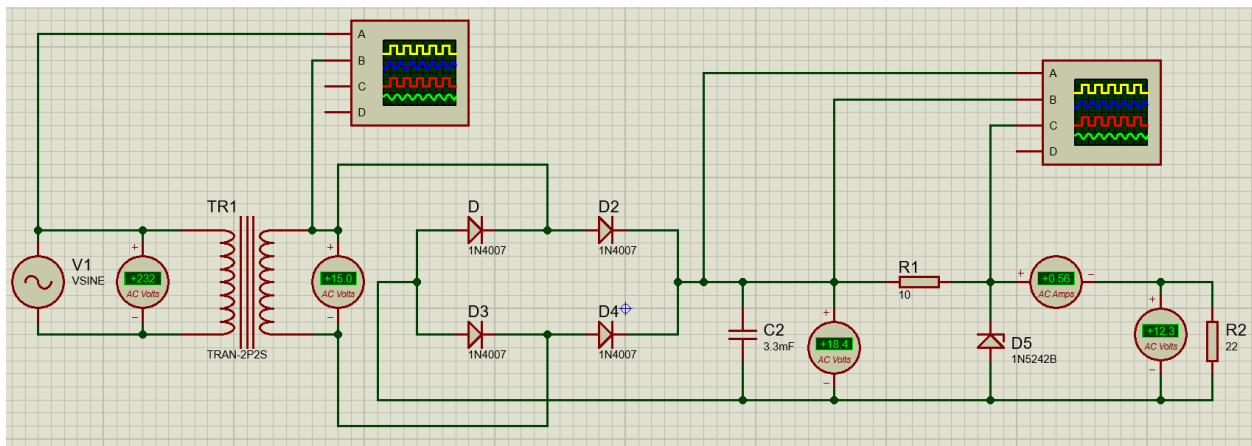


|                                  |        |
|----------------------------------|--------|
| Input Voltage of Primary Side    | 232 V  |
| Output Voltage of Secondary Side | 15 V   |
| Output Voltage                   | 12.3 V |
| Voltage across Capacitor         | 18.4 V |
| Current across the Load          | 0.56 A |

- Oscilloscope Waveforms

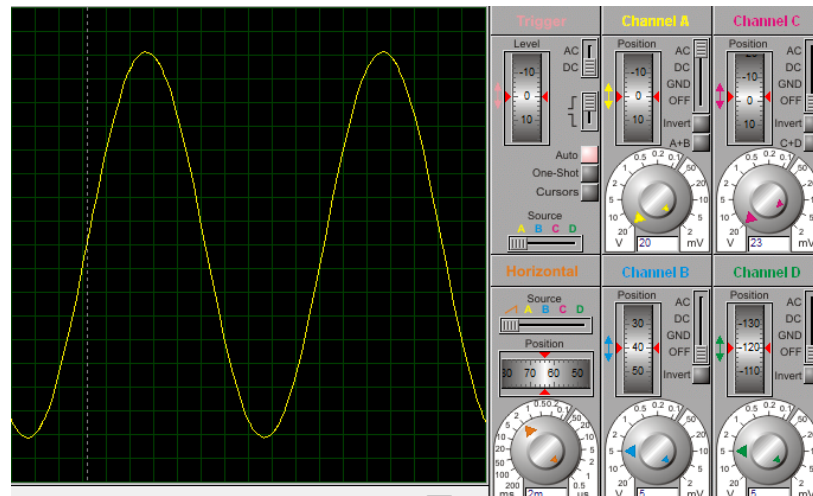


Input Waveform of Primary Side

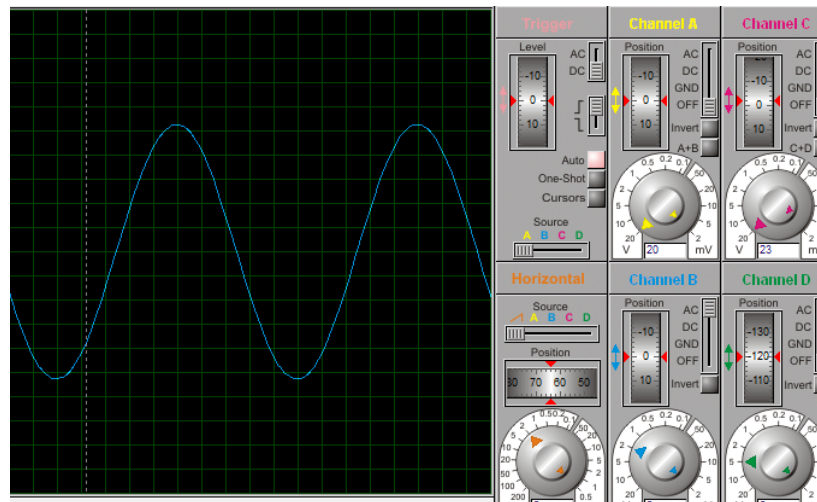


Output Waveform of Secondary Side



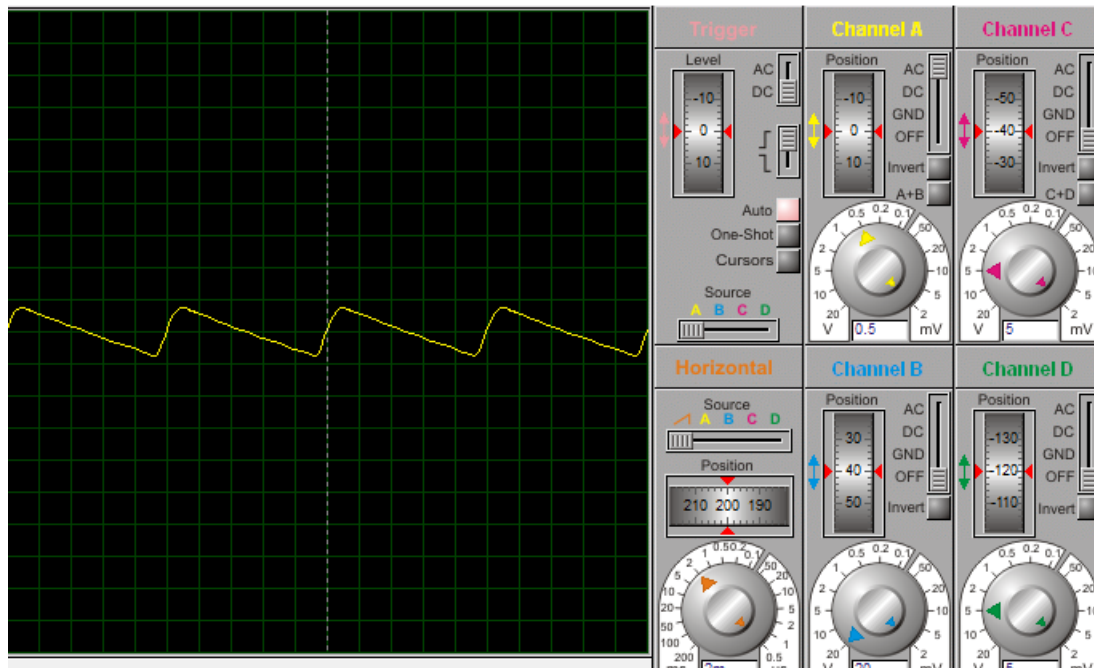


The Waveform after capacitance

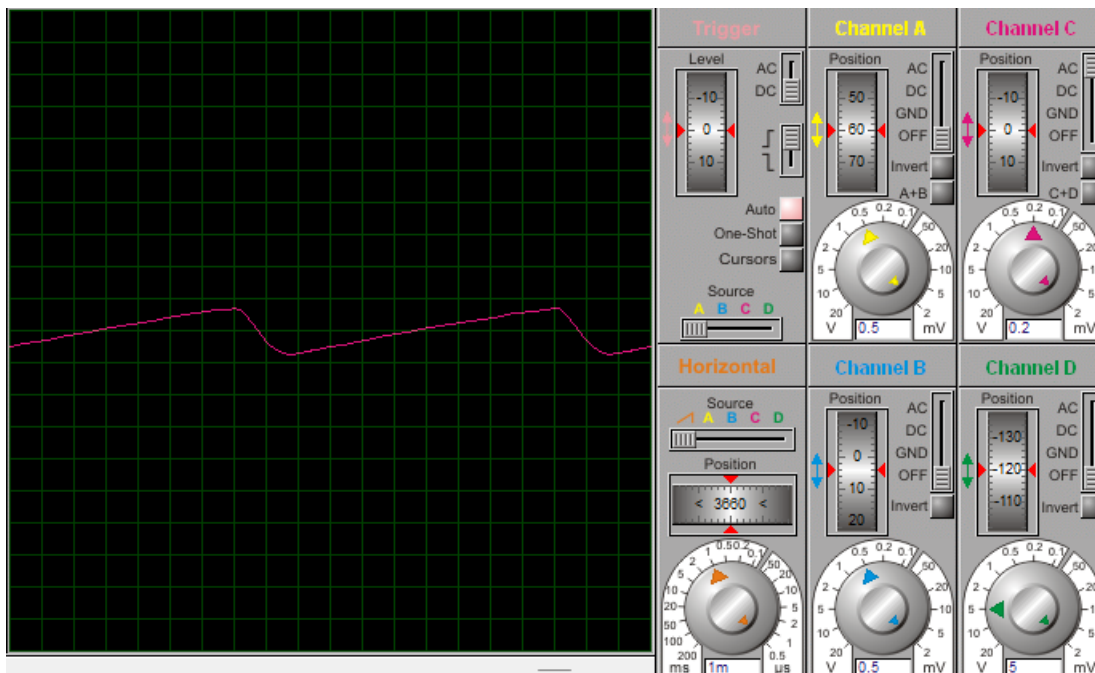


Output Waveform


➤ PCB Layout

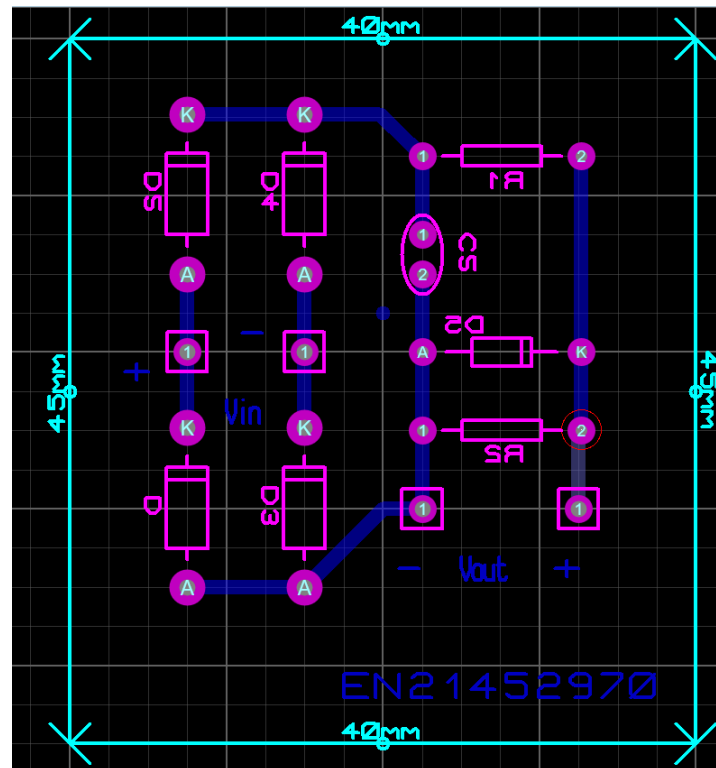

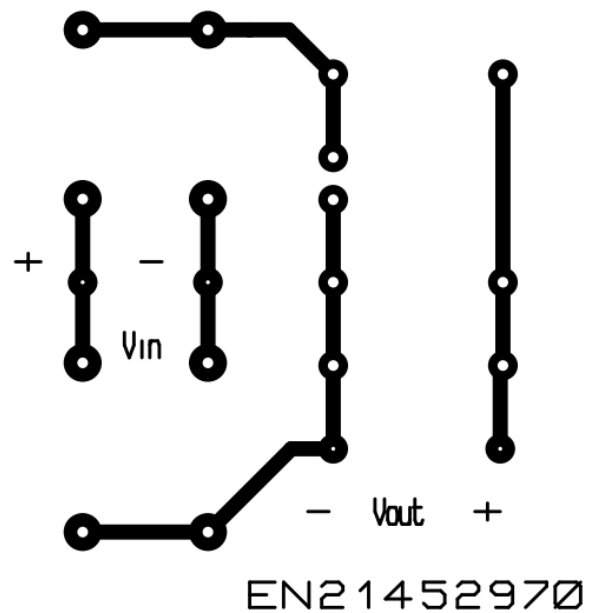- PDF type format was taken to setup the PCB.




- 3D view of circuit

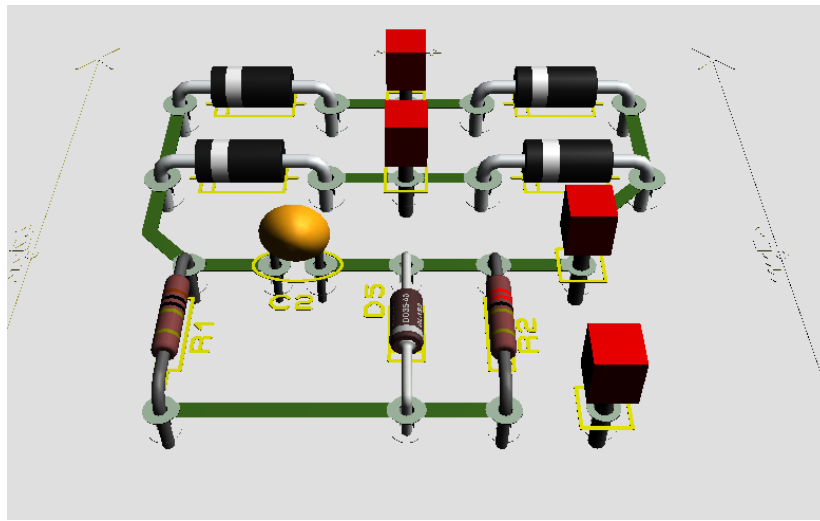
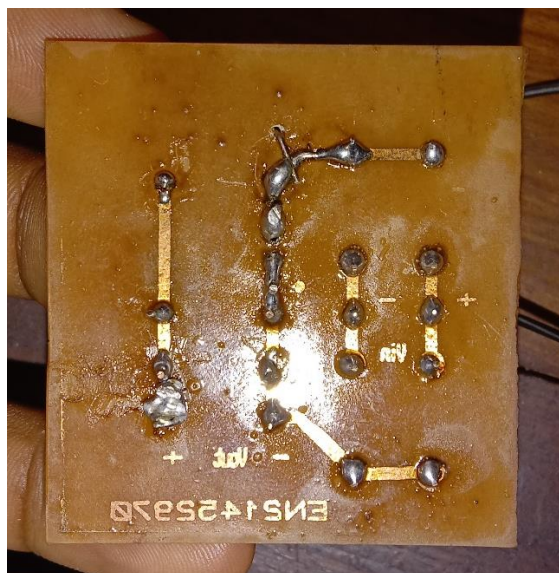
## V. Test Results


Using the proteus software, I drew the PCB layout and made the PCB first. Then, the components were soldered to the relevant places on the PCB. Also, the two input terminals of the transformer were connected to the domestic supply and the output terminal of the transformer was connected to the PCB.






- Equipment and devices used for testing
  1. Step down transformer (230V to 15V)
  2. Zener diode 12V, 1W
  3. 4 diodes of 1N4007
  4. 4.7mF capacitor
  5. 10 $\Omega$ , 22 $\Omega$  resistors
  6. Soldering iron
  7. Jumper wires
  8. PCB
  9. Multimeter

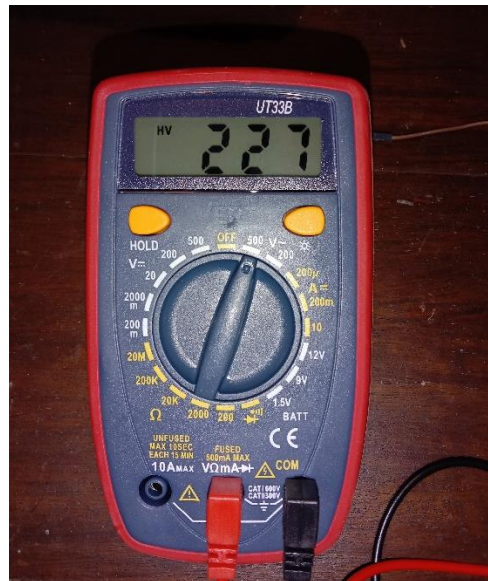
- Voltage Measurements
  - Input voltage of Transformer



- Output voltage of Transformer

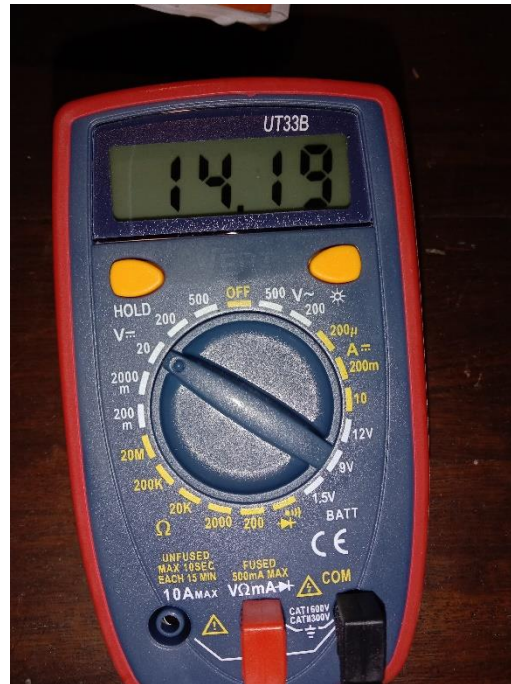


- Voltage across the capacitor

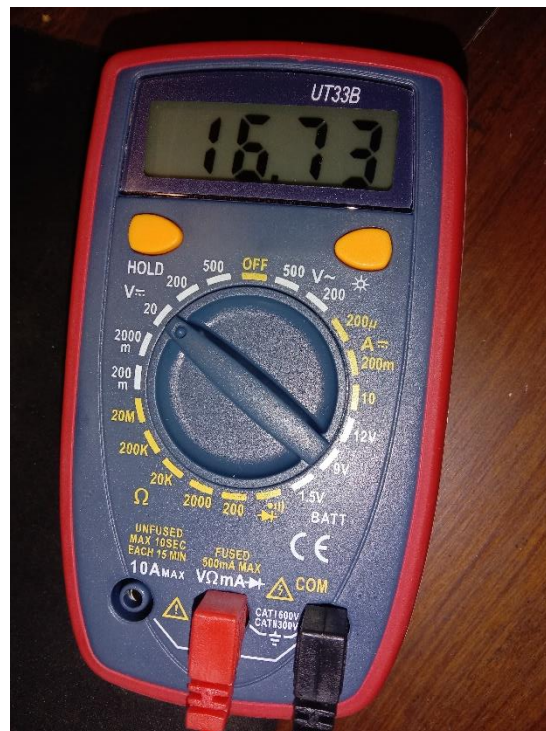




- Output Voltage

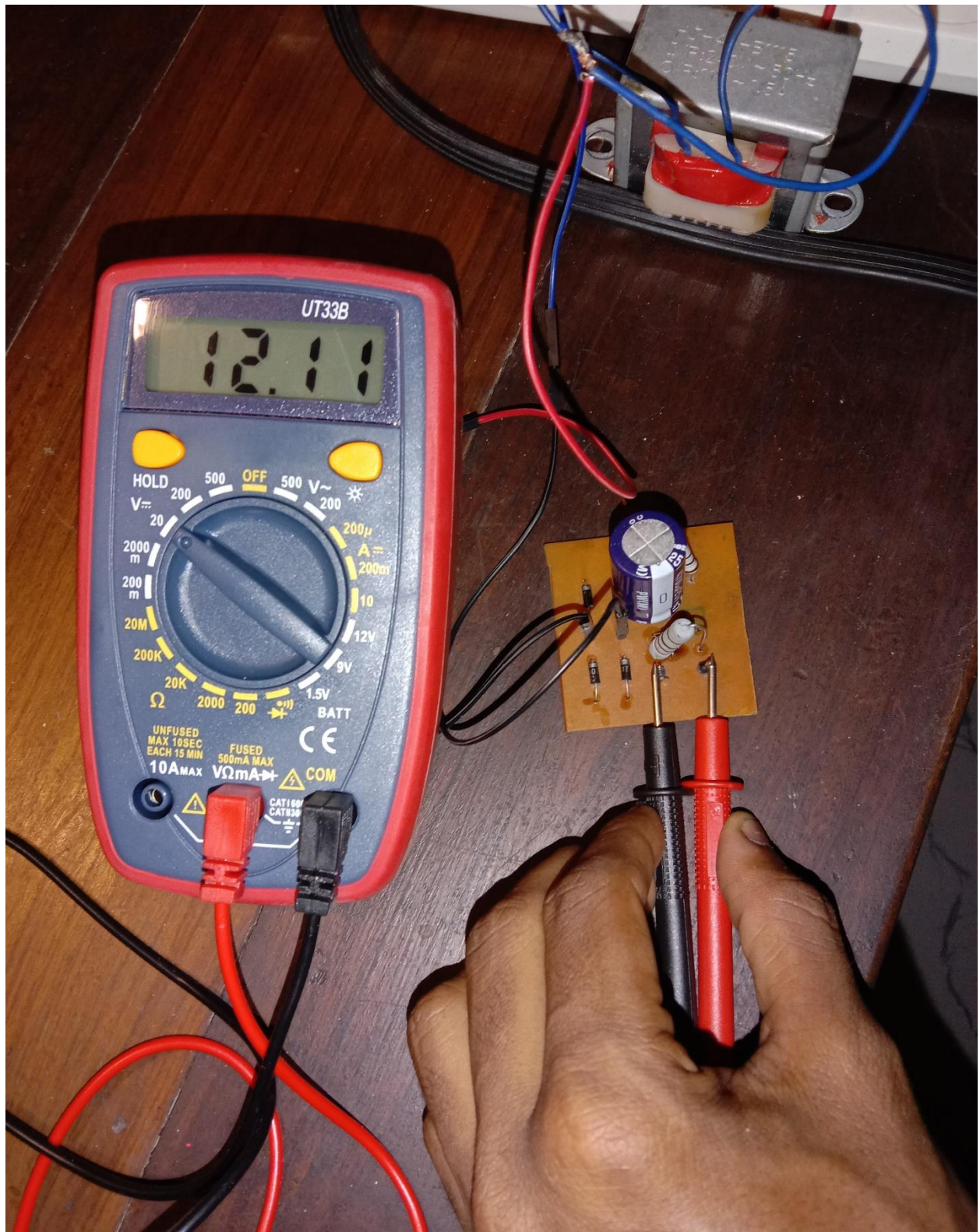




## VI. The final design

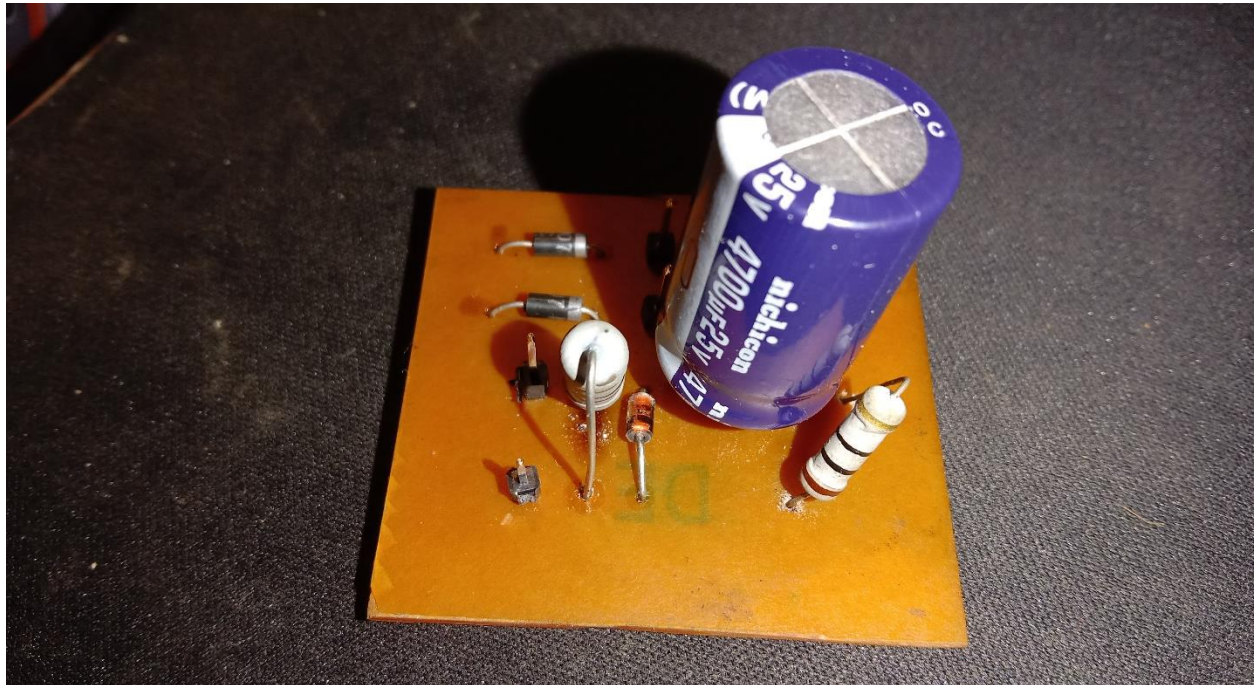



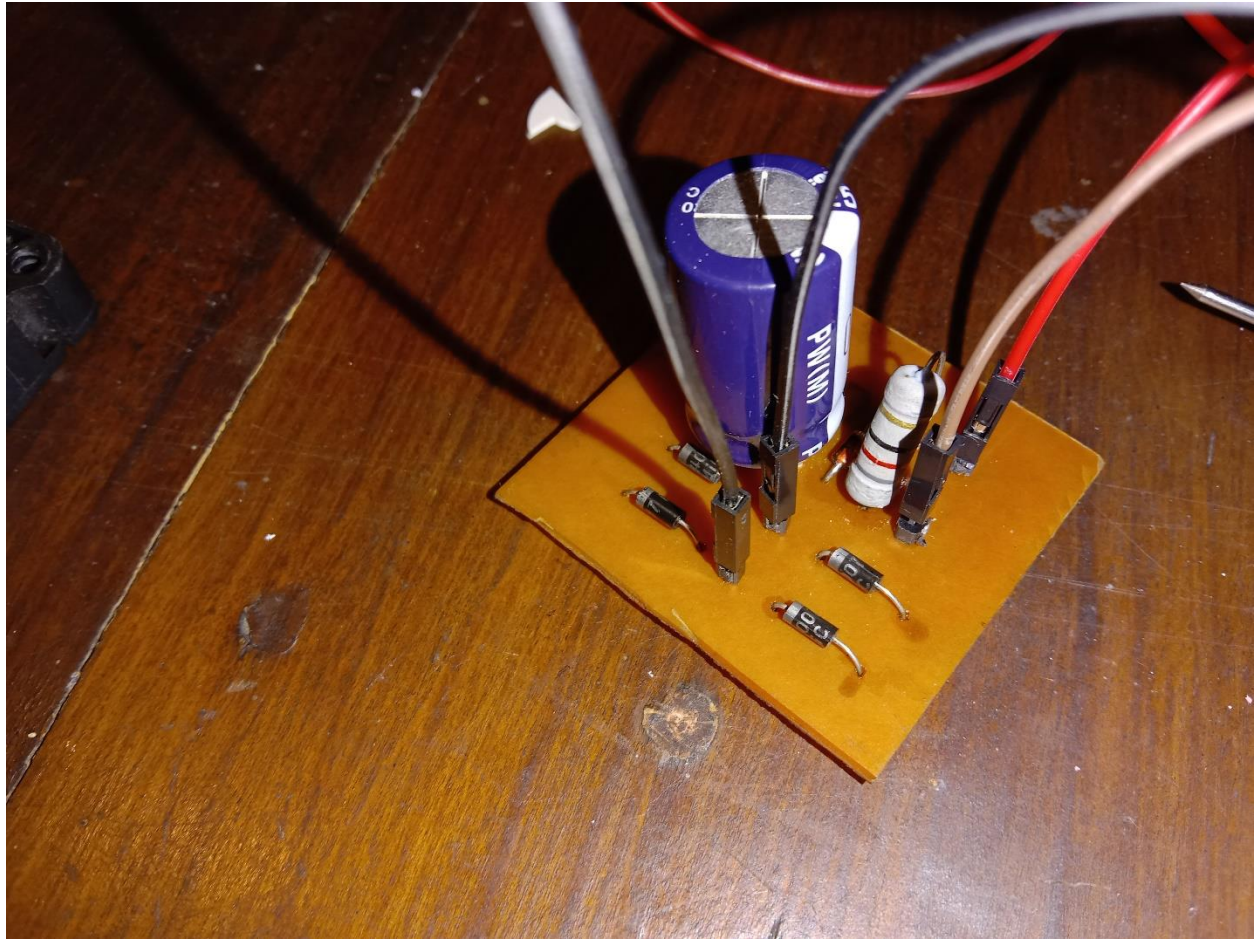

## • Discussion and Conclusion

I got to learn a lot by doing this assignment. Although these types of circuits have been designed before, this is the first time that a DC power supply has been designed. Also, it was necessary to create this circuit to do the next exam, so I created this circuit with good attention. Through this assignment, I was able to practice what I learned in class.

But many problems had to be faced while creating this. The biggest problem was to find the component related to the calculated values. It was possible to design the PCB easily. And then it was possible to solder the components related to the PCB. The next problem was that there was no transformer to supply 15V to the circuit. The solution I used for that problem was to take a 7.5V center tapped transformer and feed 15V from it to the circuit. But when the transformer was connected to the circuit and measurements were made, the desired results could not be obtained. The problem that arose while looking into it was that the transformer could not provide the amount of amperes the circuit demanded. When the circuit required more current than the related output current of the transformer, the output voltage of the transformer had dropped. Then I used a 500 mA output current transformer. Then when running the circuit everything was fine but there was one problem and that problem was that the Zener diode got a bit hot. The reason is that according to the calculations a 10W Zener diode is required, but I could find was an 1W Zener diode. But I was able to get all the desired results through this circuit.

But there were some minor differences between simulated values and practical values. In the simulated circuit, the output voltage was obtained as 12.3V. But after applying the practical circuit the value I got was 12.11 V. Although there was little difference from 12V I was very happy with this value. Because in lab3 exercise 2, when I had to get a 5V output voltage, the value I got was 5.43 V. Because this value is very close to 12V when compared to that value. A number of reasons can contribute to not being able to get 12V correctly. In the simulated circuit I gave 230V as the input voltage of the transformer but in the practical circuit I could give 227 as the transformer input voltage. Due to the same reason, the output voltage of the transformer could not be obtained as expected. It was 14.19 v. But I was able to reduce the ripple factor of the output waveform a lot. The reason for that was because I added a capacitor with a value of 4.7mF to the circuit even though the calculation indicated that a value of 3.3mF was required. So, I was able to get a much smoother DC output voltage.

And because I creatively drew the PCB layout, I was able to get a light little circuit.

I took all the results through the oscilloscope and photographed them, but due to some problem with my mobile phone, I lost all the data and lost that photos too. For this reason, I could not add the output waveform of the oscilloscope to the lab report. But I think I got everything right like the circuit and all the output values to be obtained from the circuit. So, I am happy about it and I gained a lot of experience through doing this assignment and I was very happy through this assignment.

## • References

- Anon, (n.d.). *12Volt Transformerless power supply*. [online] Available at: <https://www.elcircuit.com/2012/03/12volt-transformerless-power-supply.html> [Accessed 26 Oct. 2022].
- Email, R. by (2012). *12V Power Supply Circuits*. [online] ElectroSchematics.com. Available at: <https://www.electroschematics.com/simple-12v-dc-power-supply-circuits/> [Accessed 26 Oct. 2022].
- www.fsp-group.com. (n.d.). *AC/DC Power Supply Design in 7 Steps*. [online] Available at: <https://www.fsp-group.com/en/knowledge-tec-23.html> [Accessed 26 Oct. 2022].
- Engineer (2016). *Engineer It: How to Design the Best DC/DC Power Supply*. [online] TI Training. Available at: <https://training.ti.com/engineer-it-how-design-best-dcdc-power-supply> [Accessed 26 Oct. 2022].
- Anon, (2022). *Zener Diode Voltage Regulator / Explanation and How to Build – Wira Electrical*. [online] Available at: <https://wiraelectrical.com/zener-diode-voltage-regulator/>.

- electronicsplanet.ch. (n.d.). *E12-Series*. [online] Available at:  
<https://electronicsplanet.ch/en/resistor/e12-series.php> [Accessed 26 Oct. 2022].
  
- Kirt Blattenberger RF Cafe (n.d.). Standard Capacitor Values & Color Codes. [online]  
Available at: <https://www.rfcafe.com/references/electrical/capacitor-values.htm>.

\*\*\*\*\*